

CMPE2150 PCB Project A

AJ Armstrong

08 Dec 2024

Table of contents

Schematic Capture	1
Part 1 - KiCAD Project Setup	3
Part 2 - Schematic Sheet Setup	4
Part 3 - Place Schematic Symbols	4
Part 4 - Wire the Schematic	5
Submission	6

! Important

You should already have completed an exercise introducing and exploring KiCAD 8.0. This exercise assumes you are already familiar with the tools and interfaces of KiCAD and that you have completed a simple introductory project. If you have not done so, please complete the KiCAD introductory tutorial before proceeding with this lab assignment. On the course LMS, you should find KiCAD manuals and other guides. This document assumes you have access to those and does not go into great detail on the specifics of basic actions and functions in the application.

Schematic Capture

You are already quite familiar with schematic capture and simulation using the *NI Multisim* application used in our Electronics courses. Multisim is integrated with a PCB design package called *Ultiboard*, which students in this program have used in the past. Unfortunately, Ultiboard has an old-fashioned and perhaps overly-complicated interface, and is not commonly used in the industry. If you find yourself working with PCB design in industry, it is more likely you will work with *Altium*, *Autodesk Eagle*, or *OrCAD*. It is also increasingly likely to see the open source *KiCAD*, especially in smaller organizations unable to invest in enterprise-class products. We have selected KiCAD because it is cheap, well-maintained and multi-platform.

The reason that we have not similarly moved to KiCAD from Multisim for our electronics classes is that Multisim has a very powerful and intuitive simulation feature, which is very useful for students, especially in their first year or so of studies. KiCad also supports simulation using SPICE¹, an industry-standard platform for electronic simulation, but it is not particularly novice-friendly. More information can be found at the KiCAD site[1].

As you have read, CAD/CAM² Schematic Capture is used to formally, and in a computer-readable and -analyzeable format, the electrical circuit that you are developing. Use of standardized symbols³ and connections mean that we can easily communicate about a circuit to our colleagues—and software systems—without ambiguity. That allows us to use software to check the integrity of our design. In some cases, you will be given a design that must be imported or entered into your Schematic Capture system, and annotated to prepare for laying out a PCB to realize the design. This is the scenario we will simulate.

¹ Simulation Program with Integrated Circuit Emphasis

[1] “SPICE simulation,” *KiCad EDA*. Available: <https://www.kicad.org/discover/spice/>

² Computer-Aided Design/Computer-Aided Manufacturer

³ Both NEMA (US) and the IEC (Europe) publish standards for electrical and electronic schematics. Canadians, for the most part, use the NEMA standard.

The Circuit Design—Analog PWM Generator

The circuit we have selected for you to realize is shown below. You should also have access to an NI Multisim file for the circuit, which will allow you to see it in detail and even simulate it to investigate its behaviour.

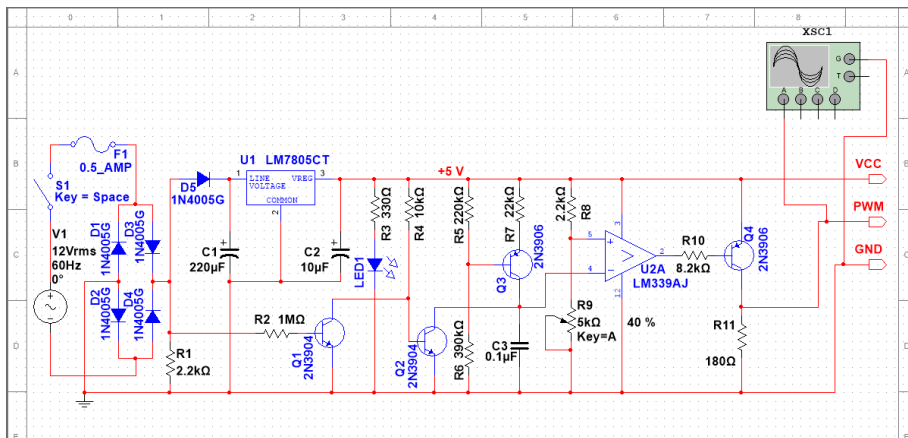


Figure 1: Analog PWM Generator

As you will recognize, this circuit is closely based on the TRIAC Dimmer circuit you analyzed and built in an earlier exercise. As you recall, the TRIAC power was controlled with an analog PWM⁴ signal whose duty cycle was controlled with a potentiometer. We have pulled out that control circuit to create slightly simpler circuit that can be used to generate a 0 to 5V TTL PWM signal with a duty cycle anywhere between 0% and 100% by adjusting a potentiometer knob.

Some significant features and changes from your earlier circuit include:

⁴ Pulse-Width Modulation

1. Obviously, the outer AC circuit driving the bulb, the bulb itself, and the TRIAC connecting the two parts of the circuit have been removed, leaving the inner PWM generation circuit.
2. The power source has been changed to 12V, as we no longer need to drive a halogen bulb, and it drops the input voltage down to a range appropriate for the simpler LM7805 regulator (U_1).
3. A power indicator LED has been added (LED_1). Note that it turns on or off depending on if the switch S_1 is toggled in the simulation.
4. The potentiometer (R_9) has been changed to $5K\Omega$, to make the range of PWM values output more smooth and linear.
5. Some output pins have been added.

Part 1 - KiCAD Project Setup

Follow the procedure below—nearly identical to the detailed one presented in the tutorial—to create your project to realize the schematic above.

Note

It is strongly recommended that you create your KiCAD project in a Github repository to track your progress, keep a backup, and foster working in multiple locations. You should find KiCAD 8.0 installed on all CNT computers.

1. Create and checkout a Github repository using whatever tool you ordinarily use, like *Github Desktop*. Remember to regularly check in your work and use *Pull* and *Push* at the beginning and end of work sessions to ensure your work is tracked and backed up. Your proof-of-work is a detailed Github history.
2. Open KiCAD 8.0 and select *File* $\rightarrow$ *New Project*. Name your project “PWMGenerator- $\langle UserID \rangle$ ”, replacing $\langle UserID \rangle$ with your NAIT username. You do not need to create a new folder if you already did so for the Github project. Then click *Save*.
3. If you have not already done so, set up the automatic project backups to your preferences. Note that it is usually unnecessary to push backups to Github, but they are nice to have for local faults and emergency recovery.
4. If you haven’t already done so, setup the Symbol Library to use the recommended option of copying the default global symbol library table.

5. For settings not mentioned above, select the defaults or use your own judgement.

Part 2 - Schematic Sheet Setup

Now, open the *Schematic Editor* and perform the following procedure:

1. Select *File* → *Page Settings* to open the sheet setup.
2. Choose a size of *8.5 x 11in* with *Landscape* orientation. Set the revision to 0. Use today's date. You'll only need one sheet. Add a title of "CMPE2150 PWM Generator - <UserID>⁵". Use "NAIT CNT" as your Company. Add your full name to the first comment. Save your work and confirm that the *Title Block* looks correct.⁶

Note

Get in the habit of incrementing the revision number every time you do a check in of a new major feature or significant update or fix. This author uses a scheme where the major revision is incremented for such significant updates, and minor revisions are incremented each *Push* to Github. Thus, Rev. 2.3 would be the third push since the second major revision. Note that you can access the Schematic Sheet properties to update the revision number or anything else by double-clicking the title.

⁵ *Mutatis mutandis*

⁶ Now would be a good time to check in your work to GitHub.

Part 3 - Place Schematic Symbols

It's finally time to start capturing our schematic. We will do this in several phases: first we will place the component symbols using the NEMA (US) symbols that you are used to. Then we will wire the schematic with connections between the components. This will be followed by choosing the values, features and appropriate footprints for our PCB realization. Finally, we will make some adjustments to the schematic to prepare it for use in creating our PCB design. Of course, as you become familiar with the tools and processes, you won't be quite so fastidious. It is common to select values and footprints, and even wire components together as we place them. While we won't stop you from doing so, beginners may find it helpful to go through this more structured phased approach.

Add the components from our schematic using the tools and techniques you learned from the tutorial. The notes below may be helpful.

1. Capture the schematic the same way we design and analyze them: left to right (input to output) and top to bottom (Vcc to GND).

2. Get used to using the hotkeys from the KiCAD cheat sheet rather than selecting buttons and menus (eg. using *A* for adding a symbol). It's much faster and more efficient once you get used to them.
3. Use the grid to align components neatly, anticipating the upcoming wired connections.
4. At this point, focus on neat placement and arrangement of the symbols. Do not bother with values and footprints until later.
5. Please use NEMA (sometimes called 'US' or 'American') symbols. The only one likely to matter is the resistors. Use the sawtooth symbol, not the rectangle (look for `_US` in the symbol name).
6. You can use "VSIN" as a search to find the power supply⁷.
7. It's helpful when finding the symbols that you want to use the various keywords that you have learned in your studies. For example, try "SPST" for the switch. You should feel free to help each other in finding symbols. Do not worry—if you get an incorrect symbol, it's relatively trivial to fix.
8. It is acceptable to use the KiCAD-generated labels and references. However, in such a case, you should be careful what order you add components to keep the numbers organized (ie. resistor numbers incrementing left to right) and make it easier to find components on the schematic.
9. Note that there are two NPN and two PNP transistors in the circuit, and the orientation of the PNPs. The mirror tool (*X* or *Y*) will be helpful
10. Two of the connections (VCC and GND) on the LM339 in Multisim do not appear in KiCAD. It is normal practice to leave those connections out in a schematic unless they are connected to sources other than the circuit's VCC and GND. You can leave them out.
11. You can use a `CONN_01x03`⁸ to get the three output pins on the right of the schematic.
12. Make sure you do a check-in (and probably a push) to GitHub when you're done this section.

⁷ But don't get too attached to it. We'll be replacing it with a barrel-jack connector soon enough.

⁸ Three-pin header row

Part 4 - Wire the Schematic

Once you have all the symbols (or suitable stand-ins) in place. Use the techniques and tools that you used in the tutorial. This is pretty straightforward, but neatness counts. Ensure that symbols are properly aligned and rotated, and that the wire routes are short, simple and neat.

Notes:

1. Add a **VCC** and **GND** net connection using power symbols (*P*), as described in the tutorial. Note that the AC source still *does not* connect to those nets. That's one thing we'll deal with in the final stage.
2. Let's also add some power symbols (*P*) for the AC power side. Use **VAC** on the top of the AC source the way you used **VCC** above, and **GNDPWR** for the bottom.
3. Add power flags (**PWR_FLG**) too all four of those for now.
4. Visually confirm that you have all the connections in the original schematic.
5. Again, remember to check in and push when you're done this stage. Remember to update the revision number.

Submission

When you have completed the above and checked and reviewed your work, increment the version number (yet again), check in and push the schematic design. Ask your instructor to review your schematic with you, and make any changes they require. When you are done (after, of course, incrementing the version number, checking in and pushing) submit the schematic.