

CMPE2150 PCB Project X

AJ Armstrong

17 May 2025

Table of contents

Part 1 - Schematic Capture	1
A - KiCAD Project Setup	2
B - Schematic Sheet Setup	3
C - Place Schematic Symbols	3
D - Wire the Schematic	4
Submission	5

! Important

You should already have completed an exercise introducing and exploring KiCAD 9.0 and worked on the CMPE2150 PCB Project. This project is a similar but smaller version of the that one, suitable for a skills check or timed exam. It assumes your familiarity with those exercises and notes and will therefore be comparatively terse. See the original project if you need more clarity on specific tasks. The steps in this exercise are broadly the same and presented in the same order as the original project.

Part 1 - Schematic Capture

The Circuit Design—Programmable Pulse Generator

The circuit we have selected for you to realize is shown below.

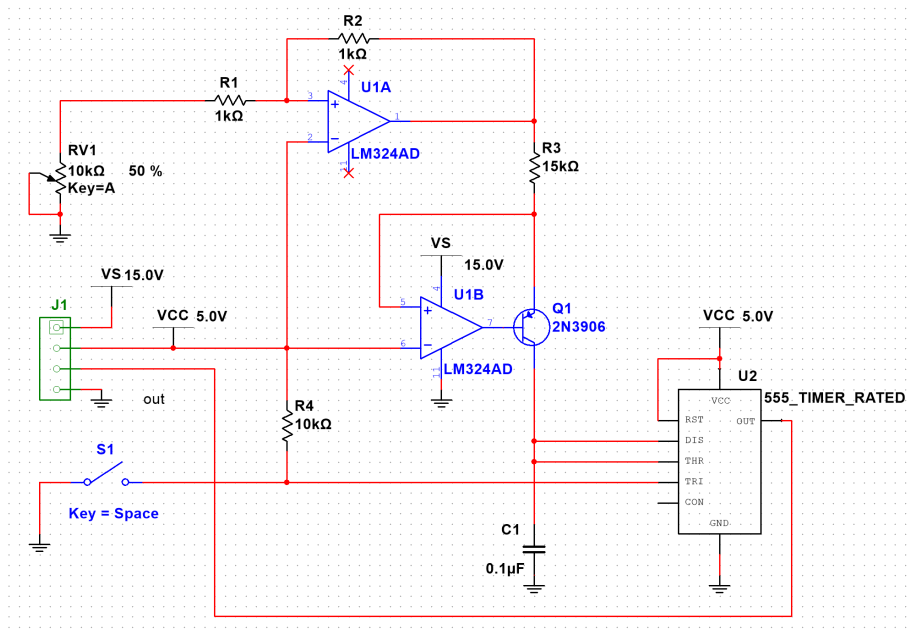


Figure 1: Programmable Pulse Generator

This circuit is from the classic *The Art of Electronics* [1, p. 242]. It is a variable width single pulse generator. The potentiometer sets the duration of the pulse and the switch triggers it.

- [1] P. Horowitz and W. Hill, *The art of electronics*, 3rd ed. Cambridge University Press, 2015.

The four-pin header represents the board's inputs and outputs:

- V_S is the voltage source to power the op amps (the top rail). It will ordinarily be $+15V_{DC}$.
- V_{cc} is the voltage source for the 555 timer and also serves as the “on” digital voltage reference. It will be $+5V_{DC}$.
- *Out* is the output of the timer. This is where the pulse generated by the circuit appears.
- *Gnd* is the ground reference for the other three pins.

A - KiCAD Project Setup

Follow the procedure below—nearly identical to the detailed one presented in the tutorial—to create your project to realize the schematic above.

1. Open KiCAD 9.0 and select *File* → *New Project*. Name your project “PulseGenerator-*<UserID>*”, replacing *<UserID>* with your NAIT username. You do not need to create a new folder if you already did so for the Github project. Then click *Save*

2. If you haven't already done so, setup the Symbol Library to use the recommended option of copying the default global symbol library table.
3. For settings not mentioned above, select the defaults or use your own judgement.

B - Schematic Sheet Setup

Now, open the *Schematic Editor* and perform the following procedure:

1. Select *File* → *Page Settings* to open the sheet setup.
2. Choose a size of *8.5 x 11in* with *Landscape* orientation. Set the revision to 0. Use today's date. You'll only need one sheet. Add a title of "CMPE2150 Pulse Generator - <UserID>¹". Use "NAIT CNT" as your Company. Add your full name to the first comment. Save your work and confirm that the *Title Block* looks correct.

¹ *Mutatis mutandis*

C - Place Schematic Symbols

Add the components from our schematic using the tools and techniques you learned from the tutorial.

1. Please use NEMA (sometimes called 'US' or 'American') symbols. The only one likely to matter is the resistors. Use the sawtooth symbol, not the rectangle (look for `_US` in the symbol name).
2. You can use a `CONN_01x04`² to get the four output pins on the left of the schematic.
3. The *Power Symbols* for this project (all sourced at the connector) are `VS`, `VCC`, and `GND`. Don't forget they'll need a *Power Flag*.

² Four-pin header row

The components in the schematic are listed below, along with a description of the component part and footprint you should use.

Note

You are not required to have the footprints completed for the first schematic checkoff. Some are included below for the sake of those of you who like to set them as you place the symbols.

Table 1: Parts List with Descriptions

Part	Reference	Footprint	Notes
Connection Header	J1	<i>See Below</i>	You'll be modifying this in a bit, so don't worry about the footprint.
Resistors	R1-R4	SMD 0805	Search terms include "R", "SMD", and "0805"
Potentiometer	RV1	<i>See Below</i>	We'll discuss this part shortly. Initially you do not need to specify a footprint.
Capacitor	C1	SMD 0805	Just an ordinary capacitor. No need for electrolytic.
Transistor	Q1	TO-92	In a real solution, you'd likely use a surface mount part, but we want to see a through-hole part, hence the TO-92 footprint.
Switch	S1	<i>See Below</i>	This will be a momentary push-button that you will select later.
Op Amps	U1A,U1B	TSSOP-14	Use an LM324 (Quad Op Amps) part to get four. Remember you'll need to deal with the two unused op amps.
Timer	U2	SOIC-8	This chip is a standard 555 timer. Use TLC555 as your search term for the part.

D - Wire the Schematic

Once you have all the symbols (or suitable stand-ins) in place, complete all the connections between components, and make the adjustments to pass the *Electrical Rules Check* without any errors or warnings.

1. Add the VS, VCC, GND net connections using power symbols (*P*).
2. Add power flags (PWR_FLG) to those three nets.

3. Place the extra op amps to one side and mark their pins as unconnected.
4. Pin 5 (*Control Voltage*) of the timer is unconnected, too.
5. Run the *Electrical Rules Check* and fix any errors or warnings.

Submission

When you have completed the above, show your clean ERC result and schematic to your instructor for checkoff.

Signature:_____